

AIM: To design 3 bit synchronous up down counter using IC7473 and JK flipflop.

Apparatus Required: 1. Electronic circuit design kit

2.IC 7473


3.Patch cords.

Theory: A **3-bit synchronous up-down counter** counts in a binary sequence from 0 to 7 and can be controlled to either increment (count up) or decrement (count down) on each clock pulse. This counter uses **IC 7473** (which contains two JK flip-flops) and an additional JK flip-flop to form the three required stages.

Key Concepts

- **Synchronous Operation:** All three flip-flops are clocked simultaneously, avoiding the delay issues in asynchronous counters.
- **Up-Down Control:** Additional control logic (usually involving AND, OR gates) is used to switch the counter between up and down modes by setting the J and K inputs appropriately.
- **Clock and Clear Inputs:** The common clock signal drives state changes across all flip-flops, while the clear input can reset the counter to zero

Logic diagram:

 

Procedure:

Step1: determine the number of flip-flops required. A 3-bit counter requires three FFs. It has 8 states (000,001,010,011,101,110,111) and all the states are valid. Hence no don't cares. For selecting up and down modes, a control or mode signal M is required. When the mode signal M=1 and counts up when M=0. The clock signal is applied to all the FFs simultaneously.

Step2: draw the state diagrams: the state diagram of the 3-bit up-down counter is drawn as

Step3: select the type of flip flop and draw the excitation table: JK flip-flops are selected and the excitation table of a 3-bit up-down counter using JK flip-flops is drawn as shown in fig

PS			mode	NS			required excitations					
Q3	Q2	Q1	M	Q3	Q2	Q1	J3	K3	J2	K2	J1	K1
0	0	0	0	1	1	1	1	x	1	x	1	x
0	0	0	1	0	0	1	0	x	0	x	1	x
0	0	1	0	0	0	0	0	x	0	x	x	1
0	0	1	1	0	1	0	0	x	1	x	x	1
0	1	0	0	0	0	1	0	x	x	1	1	x
0	1	0	1	0	1	1	0	x	x	0	1	x
0	1	1	0	0	1	0	0	x	x	0	x	1
0	1	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	1	1	x	1	1	x	1	x
1	0	0	1	1	0	1	x	0	0	x	1	x
1	0	1	0	1	0	0	x	0	0	x	x	1
1	0	1	1	1	1	0	x	0	1	x	x	1
1	1	0	0	1	0	1	x	0	x	1	1	x
1	1	0	1	1	1	1	x	0	x	0	1	x
1	1	1	0	1	1	0	x	0	x	0	x	1
1	1	1	1	0	0	0	x	1	x	1	x	1

Step 4: obtain the minimal expressions: From the excitation table we can conclude that $J_1=1$ and $K_1=1$, because all the entries for J_1 and K_1 are either X or 1. The K-maps for J_3 , K_3 , J_2 and K_2 based on the excitation table

Step5: draw the logic diagram: a logic diagram using those minimal expressions.

Result: Designed and verified Truth table of 3 bit synchronous up/down counter using IC 7473.